 


## GATE QUESTION ECE 2009 Q38

### Question

Q38) Refer to the NAND and NOR latches shown in the figure. The inputs ( $P_1, P_2$ ) for both the latches are first made (0,1) and then, after a few seconds, made (1,1). The corresponding stable outputs ( $Q_1, Q_2$ ) are:



#### Options:

- (A) NAND: first (0,1) then (0,1), NOR: first (1,0) then (0,0)
- (B) NAND: first (1,0) then (1,0), NOR: first (1,0) then (1,0)
- (C) NAND: first (1,0) then (1,0), NOR: first (1,0) then (0,0)
- (D) NAND: first (1,0) then (1,1), NOR: first (0,1) then (0,1)

### Solution

#### 1. NAND Latch Analysis

The NAND latch consists of two cross-coupled NAND gates, with outputs given by:

$$Q_1 = \overline{P_1 \cdot Q_2}, \quad Q_2 = \overline{P_2 \cdot Q_1}$$

**Step 1: Inputs (0,1)**

$$Q_1 = \overline{0 \cdot Q_2} = \overline{0} = 1$$

$$Q_2 = \overline{1 \cdot Q_1} = \overline{1} = 0$$

**Output:** ( $Q_1, Q_2$ ) = (1, 0)

**Step 2: Inputs (1,1)**

$$Q_1 = \overline{1 \cdot Q_2} = \overline{1 \cdot 0} = \overline{0} = 1$$

$$Q_2 = \overline{1 \cdot Q_1} = \overline{1 \cdot 1} = \overline{1} = 0$$

**Output:**  $(Q_1, Q_2) = (1, 0)$

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Table 1: Truth Table for NAND Gate

## 2. NOR Latch Analysis

The NOR latch consists of two cross-coupled NOR gates, with outputs given by:

$$Q_1 = \overline{P_1 + Q_2}, \quad Q_2 = \overline{P_2 + Q_1}$$

**Step 1: Inputs (0,1)**

$$Q_1 = \overline{0 + Q_2} = \overline{0} = 1$$

$$Q_2 = \overline{1 + Q_1} = \overline{1} = 0$$

**Output:**  $(Q_1, Q_2) = (1, 0)$

**Step 2: Inputs (1,1)**

$$Q_1 = \overline{1 + Q_2} = \overline{1} = 0$$

$$Q_2 = \overline{1 + Q_1} = \overline{1} = 0$$

**Output:**  $(Q_1, Q_2) = (0, 0)$

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

Table 2: Truth Table for NOR Gate

## Final Answer


- **NAND latch:** First (1,0), then (1,0) - **NOR latch:** First (1,0), then (0,0)

**Correct Option:** (C) **Truth Table for NAND and NOR Latches**

Time Step	Input $(P_1, P_2)$	NAND Latch Output $(Q_1, Q_2)$		NOR Latch Output $(Q_1, Q_2)$	
1	(0,1)	1	0	1	0
2	(1,1)	1	0	0	0

Table 3: State Table for NAND and NOR Latches
 
## Timing Diagram for NAND and NOR Latches



## Graph for NAND and NOR Latches

